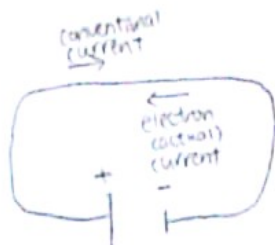


Electric Circuits: current, resistance, and power

Justin
Jung


(A)

$$I = \frac{\Delta Q}{\Delta t} \quad \left. \begin{array}{l} \uparrow \\ \text{rate of flow} \\ \text{of charge} \end{array} \right\}$$



Ohm's

$$V = IR$$

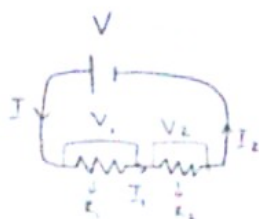


$$I = I_1 = I_2$$

$$V = V_1 + V_2 + \dots$$

$$R = R_1 + R_2 + \dots$$

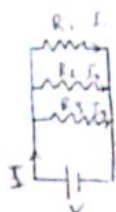higher temperature
higher resistivity
higher resistance



$$I = I_1 + I_2 + I_3$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V = V_1 = V_2 = V_3$$

$\Omega \cdot m$ (resistivity)

$\frac{PL}{A} \rightarrow m$ (length)

Ω (resistance)

m^2 (cross-sectional area)

constant; depends on material
resistivity \downarrow , conductivity \uparrow

$$R_T = R_0 [1 + \alpha_0 (T - T_0)]$$

resistance at $T^\circ C$

resistance at $20^\circ C$

constant (depends on material)

power (W)

current (A)

voltage (V)

$$P = IV$$

$$= I^2 R \rightarrow \text{resistance } (\Omega)$$

$$= \frac{V^2}{R}$$

III. ELECTRICITY AND MAGNETISM

C. Electric circuits

1. Current, resistance, power

a) Students should understand the definition of electric current, so they can relate the magnitude and direction of the current to the rate of flow of positive and negative charge.

Electric Current

↳ flow of charge through the wires of a circuit, from one terminal of the power source (battery) to the other.


• the net amount of charge that passes through the wire's full cross section at any point per unit time.

$$I = \frac{\Delta Q}{\Delta t} \leftarrow \begin{matrix} \text{change in amt of charge} \\ \text{over} \\ \text{a given time interval} \end{matrix}$$

(C/s)
⇒ ampere

The concept of Current ⇒ Conventional vs Electron

Conventional	Similarities	Electrons
<ul style="list-style-type: none"> the flow of + charge exiting from the + terminal the - terminal (not in reality's but is used to do calculations) 	<ul style="list-style-type: none"> current's magnitude is the same. 	<ul style="list-style-type: none"> electrons exit from the - side of the battery & enter the + terminal ↳ this is because electrons flow, protons don't.

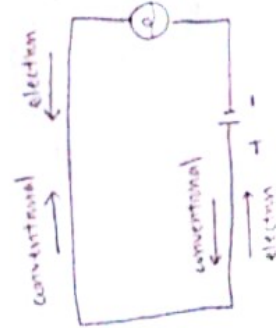

III. ELECTRICITY AND MAGNETISM

C. Electric circuits

1. Current, resistance, power

- b) Students should understand conductivity, resistivity and resistance, so they can:
- (1) Relate current and voltage for a resistor.

(Ω) resistance = $\frac{\text{voltage (V)}}{\text{current (A)}}$

$R \uparrow, I \downarrow$
 $R \downarrow, I \uparrow$

$R = \rho \frac{L}{A}$

R = resistance

L = length of wire

A = cross-sectional area of wire

$\rho = \text{resistivity } (\Omega \cdot m)$

- constant of proportionality
- depends on material used
- resistivity \downarrow , conductivity \uparrow


Resistance in...

Parallel



$\frac{1}{\Sigma R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$
 $I = I_1 + I_2 + I_3$
 $V_1 = V_2 = V_3$

Series

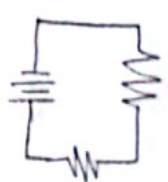

$\Sigma R = R_1 + R_2 + R_3$
 $I_1 = I_2 = I_3$
 $\Sigma V = V_1 + V_2 + V_3$

III. ELECTRICITY AND MAGNETISM

C. Electric circuits

1. Current, resistance, power


b) Students should understand conductivity, resistivity and resistance, so they can:
(3) Describe how the resistance of a resistor depends upon its length and cross-sectional area, and apply this result in comparing current flow in resistors of different material or different geometry.

$R = \rho \frac{L}{A}$ (measured in Ω)

L: length

A: cross-sectional area

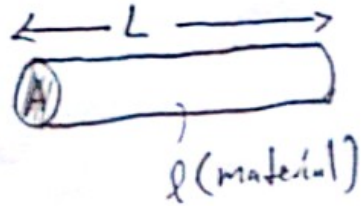ρ : coefficient of resistivity
(higher for insulators than semiconductors than conductors)



L, R, T

A, R, L



ρ , T, R, T

III. ELECTRICITY AND MAGNETISM

C. Electric circuits

1. Current, resistance, power

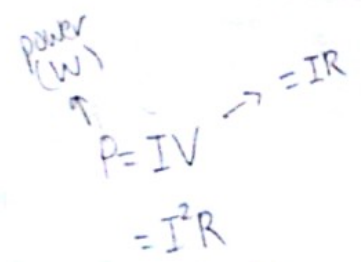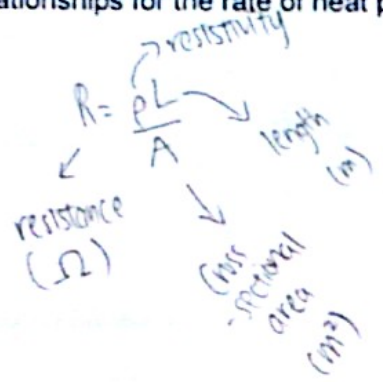- b) Students should understand conductivity, resistivity and resistance, so they can:
- (6) Apply the relationships for the rate of heat production in a resistor.



↳ the greater the resistance, the greater the rate of heat production (aka. power)

higher temperature \rightarrow higher resistivity \rightarrow higher resistance

- R \propto L
- R \propto $\frac{1}{A}$
- R \propto ρ